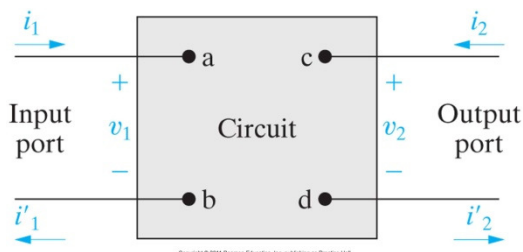


Chapter 18: Two-Port Circuits

The two-port model is used to describe the performance of a circuit in terms of the voltage and current at its input and output ports.



Model Restrictions

- No independent sources are inside the circuit between the ports (dependent can be)
- No energy is stored inside the circuit between the ports
- The current into the port is equal to the current out of the port $i_1 = i'_1$ & $i_2 = i'_2$
- No external connections exist between the input and output ports


Thus for a two-port circuit only the terminal voltages and currents are of concern

18.1 The Terminal Equations

Mostly carried out in the s-domain

Current and voltage symmetries

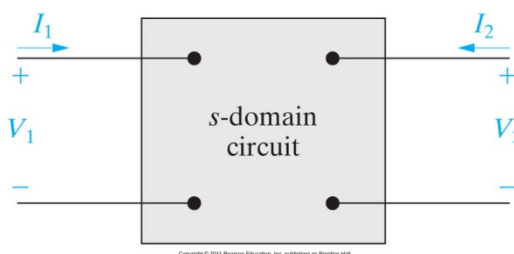- Current is directed into the top ports
- Voltages rise from lower to upper



Two of the four terminal variables (I_1, I_2, V_1, V_2) are independent therefore only two simultaneous equations are needed to describe the circuit. But there are six different ways to describe these equations.

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

$$\begin{aligned} V_1 &= a_{11}V_2 - a_{12}I_2 \\ I_1 &= a_{21}V_2 - a_{22}I_2 \end{aligned}$$

$$\begin{aligned} V_2 &= b_{11}V_1 - b_{12}I_1 \\ I_2 &= b_{21}V_1 - b_{22}I_1 \end{aligned}$$

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$

Where z, g, a, b, h and g are the **parameters** of the network.

18.2 The Two-Port Parameters

The values of a network can be determined by either computation or measurement.

To compute the z parameters:

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \Omega \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \Omega \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Omega \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \Omega$$


Measuring the z parameters

- z_{11} is the impedance seen looking into port 1 when port 2 is open
- z_{12} is a transfer impedance. It is the ratio of port 1 voltage to port 2 current when port 1 is open.
- z_{21} is a transfer impedance. It is the ratio of port 2 voltage to port 1 current when port 2 is open.
- z_{22} is the impedance seen looking into port 2 when port 1 is open

Note: each z parameter is a ratio of voltage over current and in ohms, thus its name

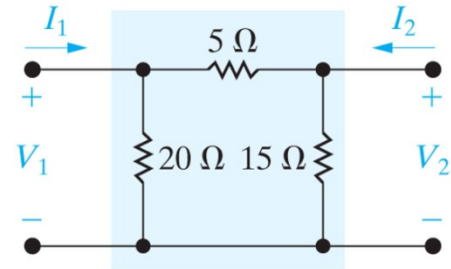Example 18.1

Find the z parameters of the following circuit.



Each of the remaining parameters can be found in a similar way.

$$\begin{aligned}
 y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0} \text{ S} & y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \text{ S} & y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0} \text{ S} & y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0} \text{ S} \\
 a_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0} & a_{12} &= -\left. \frac{V_1}{I_2} \right|_{V_2=0} \Omega & a_{21} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \text{ S} & a_{22} &= -\left. \frac{I_2}{V_2} \right|_{V_2=0} \\
 b_{11} &= \left. \frac{V_2}{I_1} \right|_{I_2=0} & b_{12} &= -\left. \frac{V_2}{I_1} \right|_{V_1=0} \Omega & b_{21} &= \left. \frac{I_1}{V_1} \right|_{I_2=0} \text{ S} & b_{22} &= -\left. \frac{I_1}{V_1} \right|_{V_1=0} \\
 h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0} \Omega & h_{12} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} & h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0} & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \text{ S} \\
 g_{11} &= \left. \frac{I_1}{V_1} \right|_{I_2=0} \text{ S} & g_{12} &= \left. \frac{I_1}{I_2} \right|_{V_1=0} & g_{21} &= \left. \frac{V_2}{V_1} \right|_{I_2=0} & g_{22} &= \left. \frac{V_2}{I_2} \right|_{V_1=0} \Omega
 \end{aligned}$$

The reciprocal set of parameters for impedance (z) and admittance (y) and called the **immittance** parameters.

The reciprocal set of parameters a and b are called the **transmission** parameters because they describe the voltage and current at one end in terms of the voltage and current at the other end.

Parameter h and g relate cross-variables input voltage and output current and output voltage to input current and are called the **hybrid** parameters.

Example 18.2 and Assessment Problems 18.1 – 18.3

Relationship between the Two-Port Parameters

TABLE 18.1 Parameter Conversion Table

$z_{11} = \frac{y_{22}}{\Delta y} = \frac{a_{11}}{a_{21}} = \frac{b_{22}}{b_{21}} = \frac{\Delta h}{h_{22}} = \frac{1}{g_{11}}$	$b_{21} = \frac{1}{z_{12}} = -\frac{\Delta y}{y_{12}} = \frac{a_{21}}{\Delta a} = \frac{h_{22}}{h_{12}} = -\frac{g_{11}}{g_{12}}$
$z_{12} = -\frac{y_{12}}{\Delta y} = \frac{\Delta a}{a_{21}} = \frac{1}{b_{21}} = \frac{h_{12}}{h_{22}} = -\frac{g_{12}}{g_{11}}$	$b_{22} = \frac{z_{11}}{z_{12}} = \frac{y_{22}}{y_{12}} = \frac{a_{11}}{\Delta a} = \frac{\Delta h}{h_{12}} = -\frac{1}{g_{12}}$
$z_{21} = \frac{-y_{21}}{\Delta y} = \frac{1}{a_{21}} = \frac{\Delta b}{b_{21}} = -\frac{h_{21}}{h_{22}} = \frac{g_{21}}{g_{11}}$	$h_{11} = \frac{\Delta z}{z_{22}} = \frac{1}{y_{11}} = \frac{a_{12}}{a_{22}} = \frac{b_{12}}{b_{11}} = \frac{g_{22}}{\Delta g}$
$z_{22} = \frac{y_{11}}{\Delta y} = \frac{a_{22}}{a_{21}} = \frac{b_{11}}{b_{21}} = \frac{1}{h_{22}} = \frac{\Delta g}{g_{11}}$	$h_{12} = \frac{z_{12}}{z_{22}} = -\frac{y_{12}}{y_{11}} = \frac{\Delta a}{a_{22}} = \frac{1}{b_{11}} = -\frac{g_{12}}{\Delta g}$
$y_{11} = \frac{z_{22}}{\Delta z} = \frac{a_{22}}{a_{12}} = \frac{b_{11}}{b_{12}} = \frac{1}{h_{11}} = \frac{\Delta g}{g_{22}}$	$h_{21} = -\frac{z_{21}}{z_{22}} = \frac{y_{21}}{y_{11}} = -\frac{1}{a_{22}} = -\frac{\Delta b}{b_{11}} = -\frac{g_{21}}{\Delta g}$
$y_{12} = -\frac{z_{12}}{\Delta z} = -\frac{\Delta a}{a_{12}} = -\frac{1}{b_{12}} = -\frac{h_{12}}{h_{11}} = \frac{g_{12}}{g_{22}}$	$h_{22} = \frac{1}{z_{22}} = \frac{\Delta y}{y_{11}} = \frac{a_{21}}{a_{22}} = \frac{b_{21}}{b_{11}} = \frac{g_{11}}{\Delta g}$
$y_{21} = -\frac{z_{21}}{\Delta z} = -\frac{1}{a_{12}} = -\frac{\Delta b}{b_{12}} = \frac{h_{21}}{h_{11}} = -\frac{g_{21}}{g_{22}}$	$g_{11} = \frac{1}{z_{11}} = \frac{\Delta y}{y_{22}} = \frac{a_{21}}{a_{11}} = \frac{b_{21}}{b_{22}} = \frac{h_{22}}{\Delta h}$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


TABLE 18.1 Parameter Conversion Table

$y_{22} = \frac{z_{11}}{\Delta z} = \frac{a_{11}}{a_{12}} = \frac{b_{22}}{b_{12}} = \frac{\Delta h}{h_{11}} = \frac{1}{g_{22}}$	$g_{12} = -\frac{z_{12}}{z_{11}} = \frac{y_{12}}{y_{22}} = -\frac{\Delta a}{a_{11}} = -\frac{1}{b_{22}} = -\frac{h_{12}}{\Delta h}$
$a_{11} = \frac{z_{11}}{z_{21}} = -\frac{y_{22}}{y_{21}} = \frac{b_{22}}{\Delta b} = -\frac{\Delta h}{h_{21}} = \frac{1}{g_{21}}$	$g_{21} = \frac{z_{21}}{z_{11}} = -\frac{y_{21}}{y_{22}} = \frac{1}{a_{11}} = \frac{\Delta b}{b_{22}} = -\frac{h_{21}}{\Delta h}$
$a_{12} = \frac{\Delta z}{z_{21}} = -\frac{1}{y_{21}} = \frac{b_{12}}{\Delta b} = -\frac{h_{11}}{h_{21}} = \frac{g_{22}}{g_{21}}$	$g_{22} = \frac{\Delta z}{z_{11}} = \frac{1}{y_{22}} = \frac{a_{12}}{a_{11}} = \frac{b_{12}}{b_{22}} = \frac{h_{11}}{\Delta h}$
$a_{21} = \frac{1}{z_{21}} = -\frac{\Delta y}{y_{21}} = \frac{b_{21}}{\Delta b} = -\frac{h_{22}}{h_{21}} = \frac{g_{11}}{g_{21}}$	$\Delta z = z_{11}z_{22} - z_{12}z_{21}$
$a_{22} = \frac{z_{22}}{z_{21}} = -\frac{y_{11}}{y_{21}} = \frac{b_{11}}{\Delta b} = -\frac{1}{h_{21}} = \frac{\Delta g}{g_{21}}$	$\Delta y = y_{11}y_{22} - y_{12}y_{21}$
$b_{11} = \frac{z_{22}}{z_{12}} = -\frac{y_{11}}{y_{12}} = \frac{a_{22}}{\Delta a} = \frac{1}{h_{12}} = -\frac{\Delta g}{g_{12}}$	$\Delta a = a_{11}a_{22} - a_{12}a_{21}$
$b_{12} = \frac{\Delta z}{z_{12}} = -\frac{1}{y_{12}} = \frac{a_{12}}{\Delta a} = \frac{h_{11}}{h_{12}} = -\frac{g_{22}}{g_{12}}$	$\Delta b = b_{11}b_{22} - b_{12}b_{21}$
	$\Delta h = h_{11}h_{22} - h_{12}h_{21}$
	$\Delta g = g_{11}g_{22} - g_{12}g_{21}$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example 18.3 and Assessment Problems 18.4

Reciprocal Two-Port Circuits

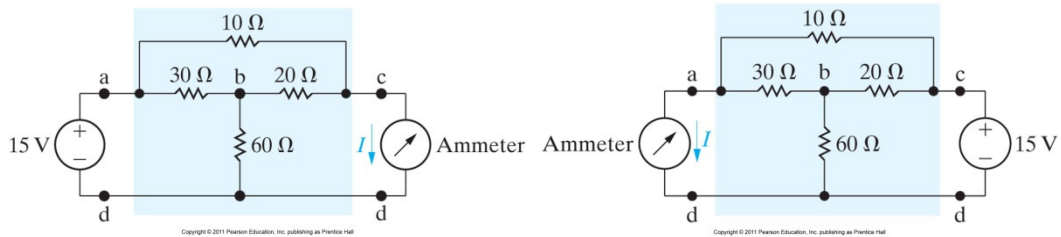

A two-port circuit is reciprocal if the interchange of an ideal voltage source at one port with an ideal ammeter at the other port produces the same ammeter reading.

A two-port circuit is also a reciprocal if the interchange of an ideal current source at one port with an ideal voltmeter at the other port produces the same voltmeter reading.


Relationships for a reciprocal two-port circuit

$$\begin{aligned} z_{12} &= z_{21} & a_{11}a_{22} - a_{12}a_{21} &= \Delta a = 1 & h_{12} &= -h_{21} \\ y_{12} &= y_{21} & b_{11}b_{22} - b_{12}b_{21} &= \Delta b = 1 & g_{12} &= -g_{21} \end{aligned}$$

A two-port circuit is symmetric if its ports can be interchanged without disturbing the values of the terminal currents and voltages.

Relationships for a symmetric two-port circuit
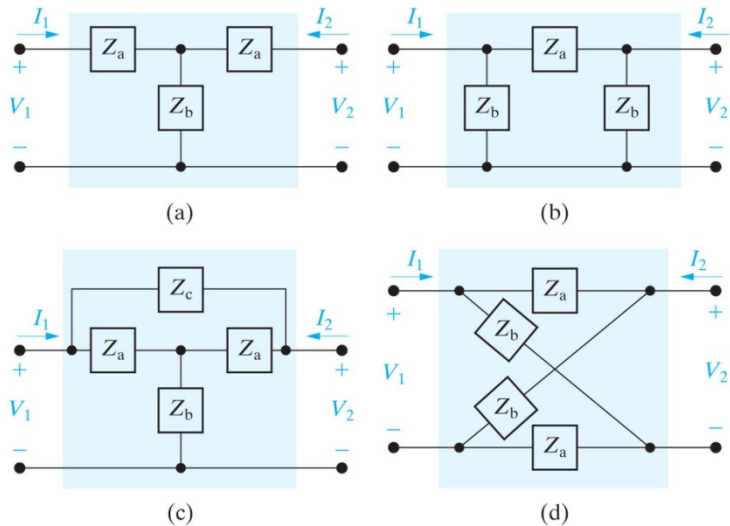
$$\begin{aligned} z_{11} &= z_{22} \\ y_{11} &= y_{22} \\ a_{11} &= a_{22} \\ b_{11} &= b_{22} \\ h_{11}h_{22} - h_{12}h_{21} &= \Delta h = 1 \\ g_{11}g_{22} - g_{12}g_{21} &= \Delta g = 1 \end{aligned}$$




Assessment Problem 18.5

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

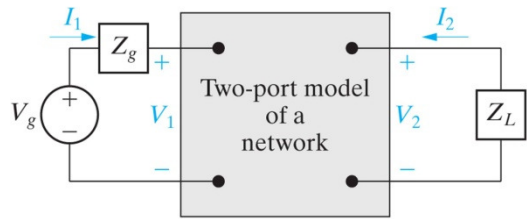18.3 Analysis of the Terminated Two-Port Circuit

Typical two-port circuits are driven in port 1 and loaded on port 2.

Where V_g & Z_g are the voltage and impedance of the source. Z_L is the load impedance.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


6 characteristics of a terminated two-port circuit

- Input impedance $Z_{in} = V_1 / I_1$ or the admittance $Y_{in} = I_1 / V_1$
- The output current I_2
- The Thevenin voltage and impedance (V_{Th} & Z_{Th}) with respect to port 2
- The current gain I_2 / I_1
- The voltage gain V_2 / V_1
- The voltage gain V_2 / V_g

See the following page for the appropriate equations

Example 18.4

Assessment Problem 18.6

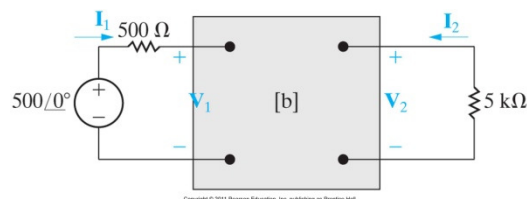

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

TABLE 18.2 Terminated Two-Port Equations

z Parameters

$$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$$

$$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

$$V_{Th} = \frac{z_{21}}{z_{11} + Z_g}V_g$$

$$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$$

$$\frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + Z_L}$$

$$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$$

$$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

y Parameters

$$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$$

$$I_2 = \frac{y_{21}V_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta yZ_gZ_L}$$

$$V_{Th} = \frac{-y_{21}V_g}{y_{22} + \Delta yZ_g}$$

$$Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta yZ_g}$$

$$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta yZ_L}$$

$$\frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{y_{21}Z_L}{y_{12}y_{21}Z_gZ_L - (1 + y_{11}Z_g)(1 + y_{22}Z_L)}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

TABLE 18.2 Terminated Two-Port Equations

a Parameters

$$Z_{in} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$$

$$I_2 = \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_gZ_L + a_{22}Z_g}$$

$$V_{Th} = \frac{V_g}{a_{11} + a_{21}Z_g}$$

$$Z_{Th} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g}$$

$$\frac{I_2}{I_1} = \frac{-1}{a_{21}Z_L + a_{22}}$$

$$\frac{V_2}{V_1} = \frac{Z_L}{a_{11}Z_L + a_{12}}$$

$$\frac{V_2}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$$

b Parameters

$$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$$

$$I_2 = \frac{-V_g\Delta b}{b_{11}Z_g + b_{21}Z_gZ_L + b_{22}Z_L + b_{12}}$$

$$V_{Th} = \frac{V_g\Delta b}{b_{22} + b_{21}Z_g}$$

$$Z_{Th} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}}$$

$$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$$

$$\frac{V_2}{V_1} = \frac{\Delta bZ_L}{b_{12} + b_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{\Delta bZ_L}{b_{12} + b_{11}Z_g + b_{22}Z_L + b_{21}Z_gZ_L}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

TABLE 18.2 Terminated Two-Port Equations

h Parameters

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_L}{1 + h_{22}Z_L}$$

$$I_2 = \frac{h_{21}V_g}{(1 + h_{22}Z_L)(h_{11} + Z_g) - h_{12}h_{21}Z_L}$$

$$V_{Th} = \frac{-h_{21}V_g}{h_{22}Z_g + \Delta h}$$

$$Z_{Th} = \frac{Z_g + h_{11}}{h_{22}Z_g + \Delta h}$$

$$\frac{I_2}{I_1} = \frac{h_{21}}{1 + h_{22}Z_L}$$

$$\frac{V_2}{V_1} = \frac{-h_{21}Z_L}{\Delta hZ_L + h_{11}}$$

$$\frac{V_2}{V_g} = \frac{-h_{21}Z_L}{(h_{11} + Z_g)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$$

g Parameters

$$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$$

$$I_2 = \frac{-g_{21}V_g}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$

$$V_{Th} = \frac{g_{21}V_g}{1 + g_{11}Z_g}$$

$$Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_g}{1 + g_{11}Z_g}$$

$$\frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$$

$$\frac{V_2}{V_1} = \frac{g_{21}Z_L}{g_{22} + Z_L}$$

$$\frac{V_2}{V_g} = \frac{g_{21}Z_L}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

18.4 Interconnected Two-Port Circuits

5 ways to connect two-port circuits

- Cascade (a-param)
- Series (z-param)
- Parallel (y-param)
- Series-Parallel (h-param)
- Parallel-Series (g-param)

We will focus on the cascade connection:

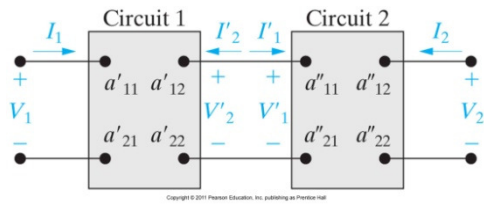

Where a' indicates first circuit.
 a'' the second.

V'_2 and I'_2 are the inputs to the second circuit V'_1 and I'_1

The new a-parameters become

$$a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21}$$

$$a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21}$$




$$a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22}$$

$$a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22}$$

If more than two units are connected in cascade, the a-parameters of the equivalent two-port circuit are found by successively reducing the circuits one pair at a time.

Example 18.5

Assessment Problem 18.7

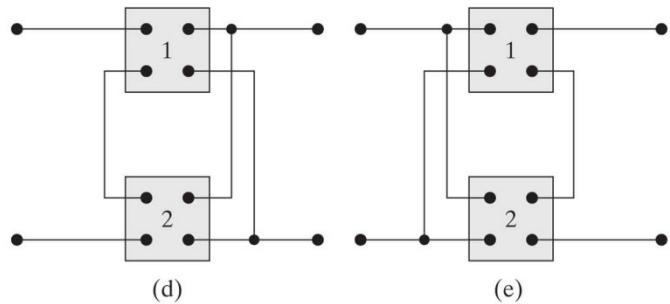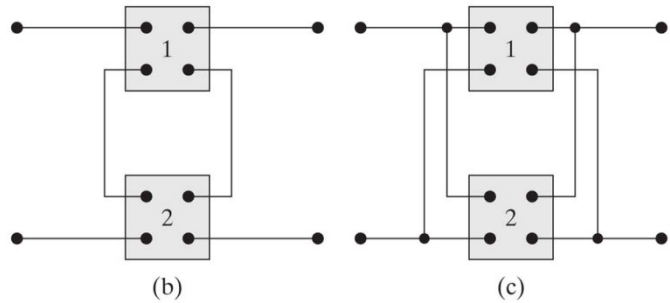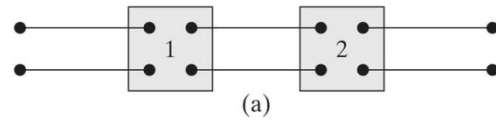

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

