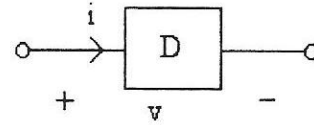



Power & the Passive Sign Convention [PSC]

Power into a device [or absorbed by the device]: $p_{in} = v i$
 [using the passive sign convention]



Power to a resistor: $p_R = v i = i^2 R = \frac{v^2}{R}$

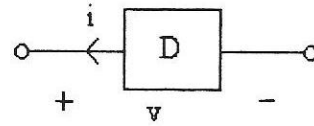Power out of a device [or delivered by the device]: $p_{out} = v i$
 [not using the passive sign convention]



Kirchhoff's Laws

KVL: algebraic sum of voltages around a loop equals zero. $\sum v = 0$; sum of all voltage drops around a loop equals zero. $p = \frac{dw}{dt}$

KCL: algebraic sum of currents at a node equals zero; or sum of all currents leaving a node equals zero.

Series & Parallel Combinations

Voltage sources: in series: add the voltage waveforms
 in parallel: the voltages must be the same

Resistance in Parallel

$$\frac{1}{R_{eq}} = \sum_{i=1}^k \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}$$

Current sources: in parallel: add the current waveforms
 in series: the currents must be the same

ADD resistances in SERIES

$$R_{eq} = \sum_{i=1}^k R_i = R_1 + R_2 + \dots + R_k$$

Two resistors in parallel:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


ADD conductances in PARALLEL

$$G_{eq} = \sum_{i=1}^k G_i = G_1 + G_2 + \dots + G_k$$

TABLE 1.3 Standardized Prefixes to Signify Powers of 10

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
deka	da	10
hecto	h	10^2
kilo	k	10^3
mega	M	10^6
giga	G	10^9
tera	T	10^{12}
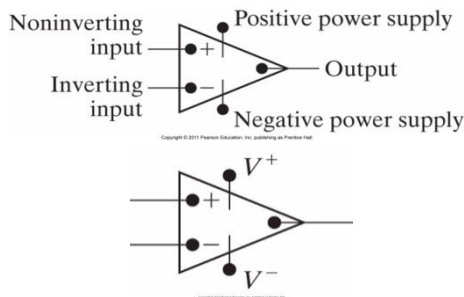
$$v = \frac{dw}{dq}; \quad i = \frac{dq}{dt}$$



Ideal Op Amps

$$V^- \leq v_o \leq V^+$$


$$i_p = i_n = 0$$

$$v_p = v_n$$

Voltage Divider

$$v_1 = i R_1 = \left(\frac{R_1}{R_1 + R_2} \right) v_s$$

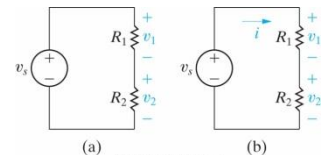
$$v_2 = i R_2 = \left(\frac{R_2}{R_1 + R_2} \right) v_s$$



Current Divider

$$i_1 = \left(\frac{R_2}{R_1 + R_2} \right) i_s$$
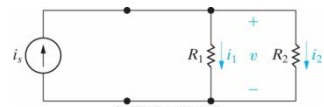
$$i_2 = \left(\frac{R_1}{R_1 + R_2} \right) i_s$$



MORE USEFUL FACTS

Method of Node Voltages:

- 1) ID nodes & select a reference node
- 2) define node voltages
- 3) write the VS equations*, using a supernode to handle a floating voltage source
- 4) write the KCL equations*
- 5) solve the equations in steps 3) & 4)

*To handle a dependent source, write the controlling signal in terms of the node voltages.

Thevenin equivalent: V_{TH} in series with R_{TH}

Norton equivalent: I_N in parallel with R_N

Equivalence relations: $R_{TH} = R_N$ & $V_{TH} = R_{TH} I_N$

Source transformation: replace a Thevenin equivalent with a Norton equivalent, or vice-versa

Method of Mesh Currents:

- 1) ID meshes
- 2) define mesh currents
- 3) write the CS equations*, using a supermesh to handle a shared current source
- 4) write the KVL equations*
- 5) solve the equations in steps 3) & 4)

*To handle a dependent source, write the controlling signal in terms of the mesh currents.

$V_{TH} = V_{OC}$ is the open circuit voltage.

$I_N = I_{SC}$ is the short circuit current.

$R_{TH} = R_N$ is the equivalent resistance.

Maximum Power Transfer:

A load resistance R_L draws maximum power from a circuit when $R_L = R_{Th}$, where R_{Th} is the Thevenin resistance of the circuit to which the load resistance is connected.

TABLE 6.1 Terminal Equations for Ideal Inductors and Capacitors

Inductors

$$v = L \frac{di}{dt} \quad (\text{V})$$

$$i = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) \quad (\text{A})$$

$$p = vi = Li \frac{di}{dt} \quad (\text{W})$$

$$w = \frac{1}{2} Li^2 \quad (\text{J})$$

Capacitors

$$v = \frac{1}{C} \int_{t_0}^t i d\tau + v(t_0) \quad (\text{V})$$

$$i = C \frac{dv}{dt} \quad (\text{A})$$

$$p = vi = Cv \frac{dv}{dt} \quad (\text{W})$$

$$w = \frac{1}{2} Cv^2 \quad (\text{J})$$

TABLE 6.2 Equations for Series- and Parallel-Connected Inductors and Capacitors

Series-Connected

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

Parallel-Connected

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Parallel Inductors Initial Current

$$i(t_0) = i_1(t_0) + i_2(t_0) + i_3(t_0) + \dots + i_n(t_0)$$

Series Capacitors Initial Voltage

$$v(t_0) = v_1(t_0) + v_2(t_0) + v_3(t_0) + \dots + v_n(t_0)$$

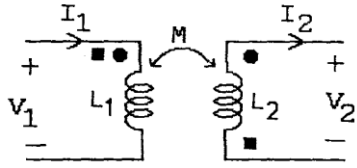Mutual Inductance and Linear Transformers



Round dots:

$$\begin{aligned} \vec{V}_1 &= j\omega L_1 \vec{I}_1 - j\omega M \vec{I}_2 \\ \vec{V}_2 &= +j\omega M \vec{I}_1 - j\omega L_2 \vec{I}_2 \end{aligned}$$

Square dots:


$$\begin{aligned} \vec{V}_1 &= j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2 \\ \vec{V}_2 &= -j\omega M \vec{I}_1 - j\omega L_2 \vec{I}_2 \end{aligned}$$

Reflected impedance $Z_r = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)]$ where $Z_{22} = R_2 + R_L + j(\omega L_2 + X_L)$

$$M = k\sqrt{L_1 L_2}$$


$$w(t) = \frac{L_1 i_1^2}{2} + \frac{L_2 i_2^2}{2} \pm i_1 i_2 M$$

Ideal Transformers

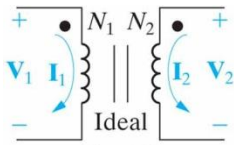


$$\begin{aligned} \frac{V_1}{N_1} &= \frac{V_2}{N_2}, \\ N_1 I_1 &= -N_2 I_2 \end{aligned}$$

(a)

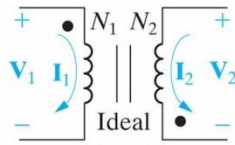


$$\begin{aligned} \frac{V_1}{N_1} &= -\frac{V_2}{N_2}, \\ N_1 I_1 &= N_2 I_2 \end{aligned}$$

(b)

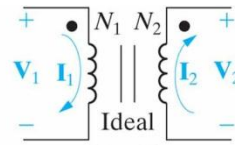

$$\begin{aligned} \frac{V_1}{N_1} &= \frac{V_2}{N_2}, \\ N_1 I_1 &= N_2 I_2 \end{aligned}$$

(c)

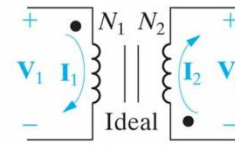


$$\begin{aligned} \frac{V_1}{N_1} &= -\frac{V_2}{N_2}, \\ N_1 I_1 &= -N_2 I_2 \end{aligned}$$

(d)

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

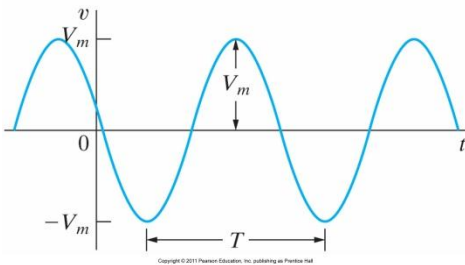The impedance seen by the source $Z_{in} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2} = \frac{1}{a^2} Z_L$ where $a = \frac{N_2}{N_1}$



$$v = V_m \cos(\omega t + \phi)$$

$$f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$V = ZI$$

$$\vec{V}_{eff} = Z \vec{I}_{eff}$$

TABLE 9.1 Impedance and Reactance Values

Circuit Element	Impedance	Reactance
Resistor	R	—
Inductor	$j\omega L$	ωL
Capacitor	$j(-1/\omega C)$	$-1/\omega C$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Rectangular to Polar conversion

$$V = A + jB = \sqrt{A^2 + B^2} \angle \left(\tan^{-1} \frac{B}{A} \right)^\circ$$

Polar to Rectangular conversion

$$V = V_m \angle \phi^\circ = V_m \cos \phi + jV_m \sin \phi$$

(Note that V_m is a magnitude and should be positive, thus angle differs)

Complex Arithmetic

Addition/Subtraction – must be in rectangular coordinates; combine real terms and imaginary terms.

$$\text{Ex. } (A_1 + jB_1) + (A_2 + jB_2) = (A_1 + A_2) + j(B_1 + B_2)$$

Multiplication – Rectangular coordinates; distribute (FOIL)

Polar coordinates; multiply the magnitudes and add the angles

Division – Rectangular coordinates; multiply the denominator and numerator by the complex conjugate of the denominator, then simplify.

Polar coordinates; divide the magnitudes and subtract the angles

Complex Number Identities $j^2 = -1$ and $\frac{1}{j} = -j$

Average Power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = V_{eff} I_{eff} \cos(\theta_v - \theta_i) = |\overrightarrow{I_{eff}}|^2 R = \frac{1}{2} I_m^2 R = \frac{|\overrightarrow{V_{eff}}|^2}{R}$$

Reactive Power

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = V_{eff} I_{eff} \sin(\theta_v - \theta_i) = |\overrightarrow{I_{eff}}|^2 X = \frac{1}{2} I_m^2 X = \frac{|\overrightarrow{V_{eff}}|^2}{X}$$

Complex power $S = P + jQ$

$$S = \frac{1}{2} V_m I_m \angle(\theta_v - \theta_i) = V_{eff} I_{eff} \angle(\theta_v - \theta_i) = \overrightarrow{V_{eff}} \overrightarrow{I_{eff}}^* = \frac{1}{2} \overrightarrow{V} \overrightarrow{I}^* = |\overrightarrow{I_{eff}}|^2 Z$$

Apparent Power $|S| = \sqrt{P^2 + Q^2}$

Power factor $\text{pf} = \cos(\theta_v - \theta_i)$

Lagging power factor: implies that the current lags the voltage – hence *inductive load*

Leading power factor: implies that the current leads the voltage – hence *capacitive load*